UNCLASSIFIED

AECD-3780

0

This report was prepared as a scientific account of Government-sponsored work. Neither the United States, nor the Commission, nor any person acting on behalf of the Commission makes any warranty or representation, express or implied, with respect to the accuracy, completeness, or usefulness of the information contained in this report, or that the use of any information, apparatus, method, or process disclosed in this report may not infringe privately owned rights. The Commission assumes no liability with respect to the use of, or from damages resulting from the use of, any information, apparatus, method, or process disclosed in this report.

UNITED STATES ATOMIC ENERGY COMMISSION

HIGH VOLTAGE RECTIFICATION

By
Walter H. Nelson

Photostat Price \$ 1-80

Microfilm Price \$ 1-80

Available from the
Office of Technical Services
Department of Commerce
Washington 25, D. C.

April 13, 1945

Tennessee Eastman Corporation
Oak Ridge, Tennessee

Technical Information Service, Oak Ridge, Tennessee

260-1

UNCLASSIFIED

DISCLAIMER

This report was prepared as an account of work sponsored by an agency of the United States Government. Neither the United States Government nor any agency Thereof, nor any of their employees, makes any warranty, express or implied, or assumes any legal liability or responsibility for the accuracy, completeness, or usefulness of any information, apparatus, product, or process disclosed, or represents that its use would not infringe privately owned rights. Reference herein to any specific commercial product, process, or service by trade name, trademark, manufacturer, or otherwise does not necessarily constitute or imply its endorsement, recommendation, or favoring by the United States Government or any agency thereof. The views and opinions of authors expressed herein do not necessarily state or reflect those of the United States Government or any agency thereof.

DISCLAIMER

Portions of this document may be illegible in electronic image products. Images are produced from the best available original document.

April 13, 1945.

copy 5-A

MEMO. ON HIGH VOLTAGE RECTIFICATIONSummary:

The conversion programs make a review of high voltage rectifier considerations timely.

The need for haste two years ago apparently forced a major departure from established design principles in rectifier circuits on this project. The tube failure rate in this plant is thus unnecessarily high. Perpetuation of this departure is preventing the design and application, by the vacuum tube industry, of kenotrons which conform with good design practice in high voltage rectification.

With new rectifier tubes now in development, a change to the circuit upon which there is complete industry agreement for high voltage application, will remove the major cause of rectifier tube failure in this plant. Almost all of the KC4 tube failures have been due to high peak inverse voltage. In addition, the mechanical failures brought about by sag of the KC4 filament against its grid helix may be largely assigned to electromechanical forces accompanying the high peak inverse voltage. The transformer bushing flashovers, occasioned by this 50,000 to 60,000 volts greater-than-necessary AC voltage for the required DC output, are responsible for considerable production outage.

The three phase full-wave circuit subjects the rectifier tubes and transformer bushings to but half the steady-state voltage impressed by the half-wave circuit, and to less than half that of the half-wave double-ye circuit on fluctuating loads. The full-wave circuit is self-damped with respect to transient oscillation voltages because a tube appears in series with every resonant circuit. This is not true in the case of the half-wave double-ye rectifier circuit as applied to the Alpha I plant. The separate emission-limited diode (562) in the C rectifier negative output lead was added, at the suggestion of the writer, when it became obvious that the rapidly varying load presented by the tank had to be isolated from the double-ye rectifier circuit for stability. As demonstrated by long use at the Coast, the full-wave circuit presents no stability problems, and its adoption will contribute flexibility to conversion designs. This flexibility could take the form of removal of the 562 and its water jacket and insulating water coil, or the application of the extra jacket to the use of two triode regulator tubes in parallel, or use of separate-tube emission limiting of the G-supply as in Alpha II. The Alpha II plant uses the full-wave circuit in the main rectifier. Space may be saved in the cubicles, because the full-wave circuit is more economical of copper than the half-wave circuit. The simple three-coil secondary of the full-wave circuit has a utilization factor of 95.5% as contrasted with 67.5% for the six-coil double-voltage secondary of the half-wave double-ye transformer.

The combination of tubes designed without conflicting requirements, with their use in the optimum rectifier circuit, will result in a minimum of high-voltage troubles, and maximum production.

CLASSIFICATION CANCELLED

DATE 11-28-55

For The Atomic Energy Commission

H. R. Canale

Chief, Declassification Branch *mce*

Page 2.

Details:

Inasmuch as the only modern radiation-cooled high-voltage kenotron immediately available two years ago was the low-current KC4, parallel operation of tubes to obtain sufficient current was necessary. It was stated by GE engineers that it would require six months to modernize the obsolete 219 kenotron which has suitable current ratings for this application. (2.5 amperes rated max., 4.5 amperes emission at rated filament voltage, at 50 kilovolts peak inverse with 450 volts drop at 1 ampere; appropriate for full-wave circuit.)

For Alpha I, GE engineers chose to parallel the KC4 tubes by means of the half-wave double-wye circuit with interphase reactor. This circuit was subsequently found so unstable with the rapidly varying loads periodically imposed by the tank that the writer's separate emission-limited diode principle was incorporated into the high voltage channels in order to isolate the rectifier from the major load disturbances. The laboratory had always used the full-wave rectifier circuit, because a survey of the literature on rectifier circuits had indicated complete agreement in the industry on design factors influencing the choice of the full-wave rectifier circuit for high-voltage applications.

The paper most pertinent to this project is one by E. V. DeBlieux, Power Transformer Engineering Department, Pittsfield Works General Electric Company, entitled "Characteristics, Design, and Applications of Rectifier Transformers." Quoting excerpts from this paper, it is shown that the "ideal rectifier circuits should have a high transformer-copper-utilization factor and should have a smooth DC voltage." "The consideration of the foregoing section indicates that the full-wave rectifier is the nearest approach to the ideal from the standpoint of utilization of transformer copper." "For radio transmitters and other circuits where a high DC voltage is required, the full-wave circuit is preferable for the following reasons:

(a) Because of the high DC voltage the loss in efficiency due to the arc drop being in series is negligible.

(b) The small capacity and/or the high voltage required usually presents a more favorable application for tubes than for metal-tank mercury-arc rectifiers.

(c) The higher the DC voltage the more difficult and costly it becomes to interlace properly the pairs of secondaries required for half-wave operation.

(d) Because of (b) and (c), full-wave operation and the resultant greater transformer copper economy can be realized."

No disadvantages are given for full-wave circuits except that they "are not suitable for use with metal-tank mercury-arc rectifiers which have only one cathode for a number of anodes." The rectifier output voltage of 50 KV used here is at present beyond the peak inverse rating of mercury-vapor tanks, so this disadvantage does not apply. Mr. DeBlieux continues:

260-3

Page 3.

"For the reasons set forth in the preceding paragraphs the half-wave rectifier circuits are preferable for power, - that it, low-voltage applications and the full-wave circuits for radio or high-voltage applications."

As pointed out in my memo. dated April 11, 1944, and another on June 20, 1944, the use of the full-wave rectifier circuit in this application presents advantages from the standpoint of behavior on transients which are as compelling as those of rectifier tube life. They are: (1) No oscillations because there are no resonant circuits which do not include a rectifier tube in series therewith. (2) Both an anode and a cathode are connected to the high end of each secondary winding so that damping of winding transients is applied to ~~either~~ polarity of surges. (3) The separate emission-limited 562 diode in Alpha I may be eliminated, or applied to useful functions in the cubicle. This diode is used in Alpha I solely because the double-wye rectifier circuit is so unstable on the rapidly-varying loads imposed by the tank that it must be isolated from them. Furthermore, the simple three-coil secondary of the full-wave circuit has a utilization factor of 95.5% as against 67.5% for the six-coil double-voltage secondary of the half-wave double-wye transformer. This permits a saving of cubicle space, as well as being more economical of copper.

Thus from the standpoint of tube life, inherent stability on load fluctuations, and continuity of operations, new tubes now in development should be designed around the optimum rectifier circuit, - the full-wave. The appended chart gives the kenotron tube situation of two years ago. It is clear that a modernized version of the 219 would have wide applications in the industry, as well as in this plant, because of its position on the chart between the group of low-current radiation-cooled kenotrons, and the higher-current water-cooled kenotrons. The advantages of avoiding plumbing and insulated water-coils are self-evident. As the 219 filament furnished 4.5 amperes emission at 22 volts, 24.5 amperes, a moderate increase in filament power will provide long life as well, when the conflicting requirement of very high peak inverse rating is avoided by the use of the full-wave rectifier circuit.

260-4

Walter H. Nelson
Walter H. Nelson,
Consultant.

WHN:pn

KENOTRONS

□ = air cooled

○ = water cooled

Original by
Walter A Nelson
300 March 1943

Copy by GINW
April 1945

Rated KV Peak Inverse Voltage

200

150

100

50

40

30

20

10

WL612

KC4

WL531

218

8020

3718

1651

219

233A

○

214

562

237A

F103A

○

222A

Rated Amps - Peak Current

.3

.4

.5

.7

1.0

2.0

3.0

5

7.5

9.1

11

0-4

4-12 OPERATIONS DIVISION
Received: 4-16-45
Entered: 4-16-45